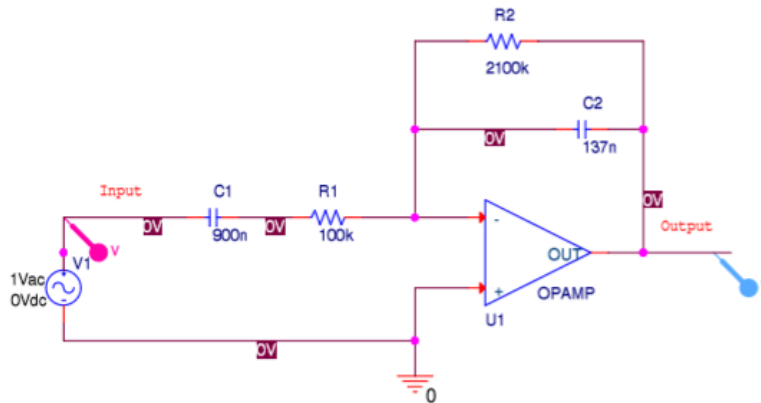


Electronics Design project 2

Laboratory 2: Practical design skills. Using PSpice in design.

Kaichun Hu 2173845H

1. Reason for the chosen component



This experiment aims to build a circuit that has a voltage gain of 5 at 1Hz and reject the mains frequency of 50Hz (i.e. have a low gain at 50Hz). And from practical restrictions, all resistance must not get larger than about $3\text{M}\Omega$ and the capacitance should not be greater than $1\mu\text{F}$.

The following values were chosen to achieve a gain of about 5 at 1Hz and low gain at 50Hz.

$C1=900\text{nF}$ $R1=100\text{k}\Omega$ $C2=137\text{nF}$ $R2=2100\text{k}\Omega$

The centre frequency is calculated using the following equation which is equal to 1Hz.

$$f = \frac{1}{2\pi \cdot \sqrt{R_1 C_1 R_2 C_2}}$$

$$\frac{1}{2 \cdot \pi \cdot \sqrt{(900 \cdot 10^{-9}) \cdot 100 \cdot 10^3 \cdot (2100 \cdot 10^3) \cdot 137 \cdot 10^{-9}}}$$

$$= 0.9890743652$$


The gain at 1Hz is calculated using the formula below and is equal to 5.

$$\text{Gain} = \frac{\sqrt{\frac{R_2^2 \cdot \frac{1}{\omega C_2}^2}{R_2^2 + \frac{1}{\omega C_2}^2}}}{\sqrt{R_1^2 + \frac{1}{\omega C_1}^2}}$$

$$\left(\frac{\sqrt{\frac{(2100 \cdot 10^3)^2 \cdot \left(\frac{1}{(2\pi \cdot 1 \cdot 137 \cdot 10^{-9})}\right)^2}}{(2100 \cdot 10^3)^2 + \left(\frac{1}{(2\pi \cdot 1 \cdot 137 \cdot 10^{-9})}\right)^2}}}{\sqrt{(100 \cdot 10^3)^2 + \left(\frac{1}{(2\pi \cdot 1 \cdot 900 \cdot 10^{-9})}\right)^2}} \right)$$

$$= 5.00375218486$$

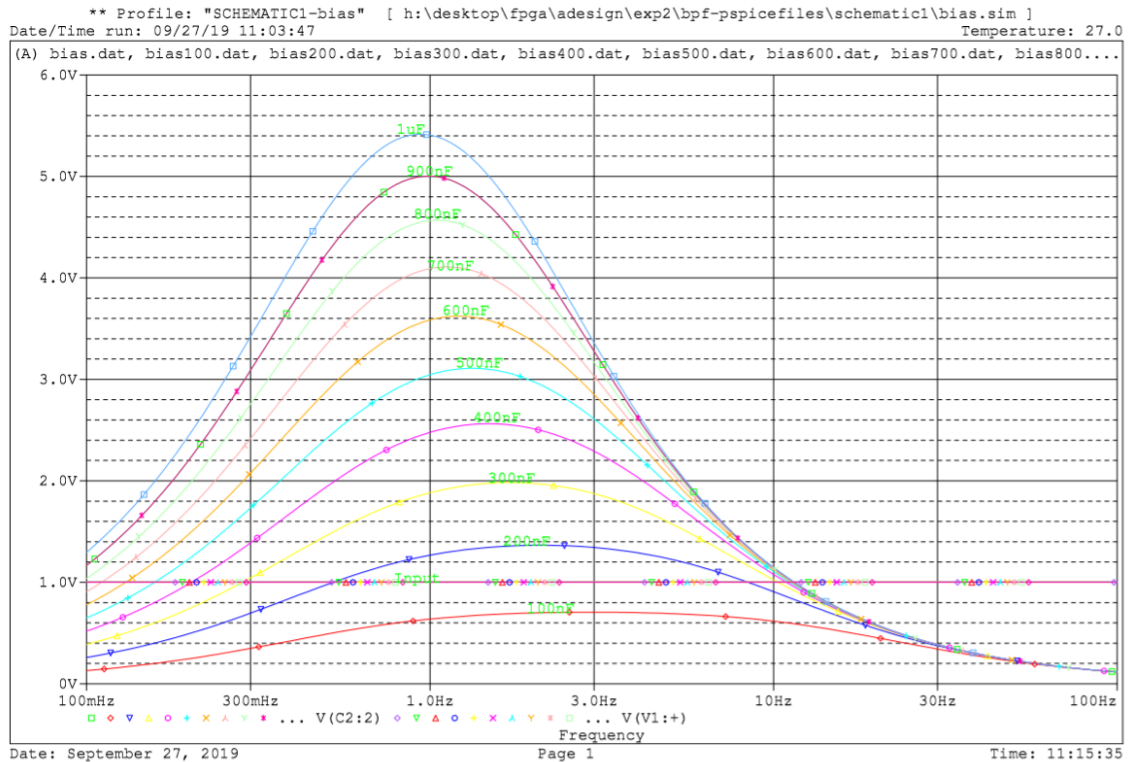2. Plot of output voltage against frequency (Including a family of curves showing how the value of C1, the input capacitor, changes the low frequency cut-off of the design.)



3. The same data with the graphs in dB

